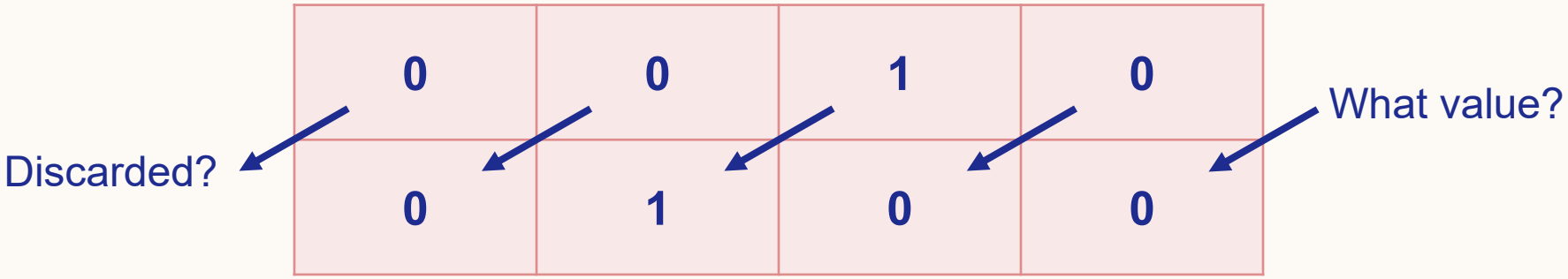
# SHIFT REGISTER

Create a circuit that will shift an 8-bit binary number. On a falling edge:

- If *load* is high, should load the value from *in*
- If *shift* is high, should load the previous value "shifted" by one place to the left




You may assume *load* and *shift* are not high at the same time…